
Digital Logic Design

Chapter 3

Gate-Level Minimization

3-1 Introduction

- ▣ Gate-level minimization refers to the design task of finding an optimal gate-level implementation of Boolean functions describing a digital circuit.

3-2 The Map Method

- Logic minimization

- ◆ Algebraic approaches: lack specific rules
- ◆ The Karnaugh map
 - » A simple straight forward procedure
 - » A pictorial form of a truth table
 - » Applicable if the number of variables < 7

- A diagram made up of squares

- ◆ Each square represents one minterm

Two-Variable Map

■ A two-variable map

- ◆ Four minterms $xy, xy', x'y, x'y'$
- ◆ $x' = \text{row } 0; x = \text{row } 1$
- ◆ $y' = \text{column } 0; y = \text{column } 1$
- ◆ A truth table in square diagram
- ◆ Fig. 3.2(a): $xy = m_3$
- ◆ Fig. 3.2(b): $m_1 + m_2 + m_3 = x'y + xy' + xy = x(y + y') + y(x + x') = x + y$

 


Figure 3.1 Two-variable Map

 


Figure 3.2 Representation of functions in the map

A Three-variable Map

■ A three-variable map (Eight minterms)

- ◆ The minterms arranged in Gray code sequence not in binary
- ◆ Any two adjacent squares (vertically or horizontally. But not diagonally) in the map differ by only one variable
 - » e.g., m_5 and m_7 can be simplified
 - » $m_5 + m_7 = xy'z + xyz = xz(y' + y) = xz$

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6

(a)

		y			
		00		01	11 10
x	yz	00	01	11	10
	0	m_0 $x'y'z'$	m_1 $x'y'z$	m_3 $x'yz$	m_2 $x'yz'$
x	1	m_4 $xy'z'$	m_5 $xy'z$	m_7 xyz	m_6 xyz'
		z			

(b)

Figure 3.3 Three-variable Map

A Three-variable Map

- ◆ m_0 and m_2 (m_4 and m_6) are adjacent
- ◆ $m_0 + m_2 = x'y'z' + x'yz' = x'z'(y' + y) = x'z'$
- ◆ $m_4 + m_6 = xy'z' + xyz' = xz'(y' + y) = xz'$

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6

(a)

		y			
		xz			
		0 0	0 1	1 1	1 0
x	0	$x'y'z'$	$x'y'z$	$x'yz$	$x'yz'$
x	1	$xy'z'$	$xy'z$	xyz	xyz'
		z			

(b)

Fig. 3-3 Three-variable Map

Example 3.1

Example 3.1: simplify the Boolean function $F(x, y, z) = \Sigma(2, 3, 4, 5)$

◆ $F(x, y, z) = \Sigma(2, 3, 4, 5) = x'y + xy'$

 


Figure 3.4 Map for Example 3.1, $F(x, y, z) = \Sigma(2, 3, 4, 5) = x'y + xy'$

Example 3.2

▣ Example 3.2: simplify $F(x, y, z) = \Sigma(3, 4, 6, 7)$

◆ $F(x, y, z) = \Sigma(3, 4, 6, 7) = yz + xz'$

 


Figure 3.5 Map for Example 3-2; $F(x, y, z) = \Sigma(3, 4, 6, 7) = yz + xz'$

Four adjacent Squares

■ Consider four adjacent squares

- ◆ $m_0 + m_2 + m_4 + m_6 = x'y'z' + x'yz' + xy'z' + xyz' = x'z'(y' + y) + xz'(y' + y) = x'z' + xz' = z'$
- ◆ $m_1 + m_3 + m_5 + m_7 = x'y'z + x'yz + xy'z + xyz = x'z(y' + y) + xz(y' + y) = x'z + xz = z$

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6

(a)

		y			
		xz		11	10
x	0	$x'y'z'$	$x'y'z$	$x'yz$	$x'yz'$
	1	$xy'z'$	$xy'z$	xyz	xyz'
		z			


(b)

Figure 3.3 Three-variable Map

 Example 3.3

▣ Example 3.3: simplify $F(x, y, z) = \Sigma(0, 2, 4, 5, 6)$

◆ $F(x, y, z) = \Sigma(0, 2, 4, 5, 6) = z' + xy'$



Note: $y'z' + yz' = z'$

Figure 3.6 Map for Example 3-3, $F(x, y, z) = \Sigma(0, 2, 4, 5, 6) = z' + xy'$

Example 3.4

■ Example 3.4: let $F = A'C + A'B + AB'C + BC$

- ◆ Express in sum of minterms and find the minimal SOP
- ◆ Note: $A'C = A'$ (first row) and C (two middle columns) to give squares 001 & 011.

Ans: $F(A, B, C) = \Sigma(1, 2, 3, 5, 7) = C + A'B$

 


Figure 3.7 Map for Example 3.4, $A'C + A'B + AB'C + BC = C + A'B$

Summary of three-variable Map

- *One square* represents one minterm, giving a term with *three literals*.
- *Two adjacent squares* represent a term with *two literals*.
- *Four adjacent squares* represent a term with *one literal*.
- *Eight adjacent squares* encompass the entire map and produce a function that is always equal to *1*.

3.3 Four-Variable Map

□ The map

- ◆ 16 minterms
- ◆ Combinations of 2, 4, 8, and 16 adjacent squares

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6
m_{12}	m_{13}	m_{15}	m_{14}
m_8	m_9	m_{11}	m_{10}

(a)

		yz		y	
		00	01	11	10
w	00	$w'x'y'z'$	$w'x'y'z$	$w'x'yz$	$w'x'yz'$
	01	$w'xy'z'$	$w'xy'z$	$w'xyz$	$w'xyz'$
	11	$wxy'z'$	$wxy'z$	$wxyz$	$wxyz'$
	10	$wx'y'z'$	$wx'y'z$	$wx'yz$	$wx'yz'$
		z			

(b)

Figure 3.8 Four-variable Map

Summary of four-variable Map

- ▣ *One square* represents one minterm, giving a term with *four literals*.
- ▣ *Two adjacent squares* represent a term with *three literals*.
- ▣ *Four adjacent squares* represent a term with *two literals*.
- ▣ *Eight adjacent squares* represent a term with *one literal*.
- ▣ *Sixteen adjacent squares* produce a function that is always equal to *1*.

Example 3.5

■ Example 3.5: simplify $F(w, x, y, z) = \Sigma(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$

 


Figure 3.9 Map for Example 3-5; $F(w, x, y, z) = \Sigma(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14) = y' + w'z' + xz'$

3.4 Five-Variable Map

- Map for more than four variables becomes complicated
 - ◆ Five-variable map: two four-variable map (one on the top of the other).

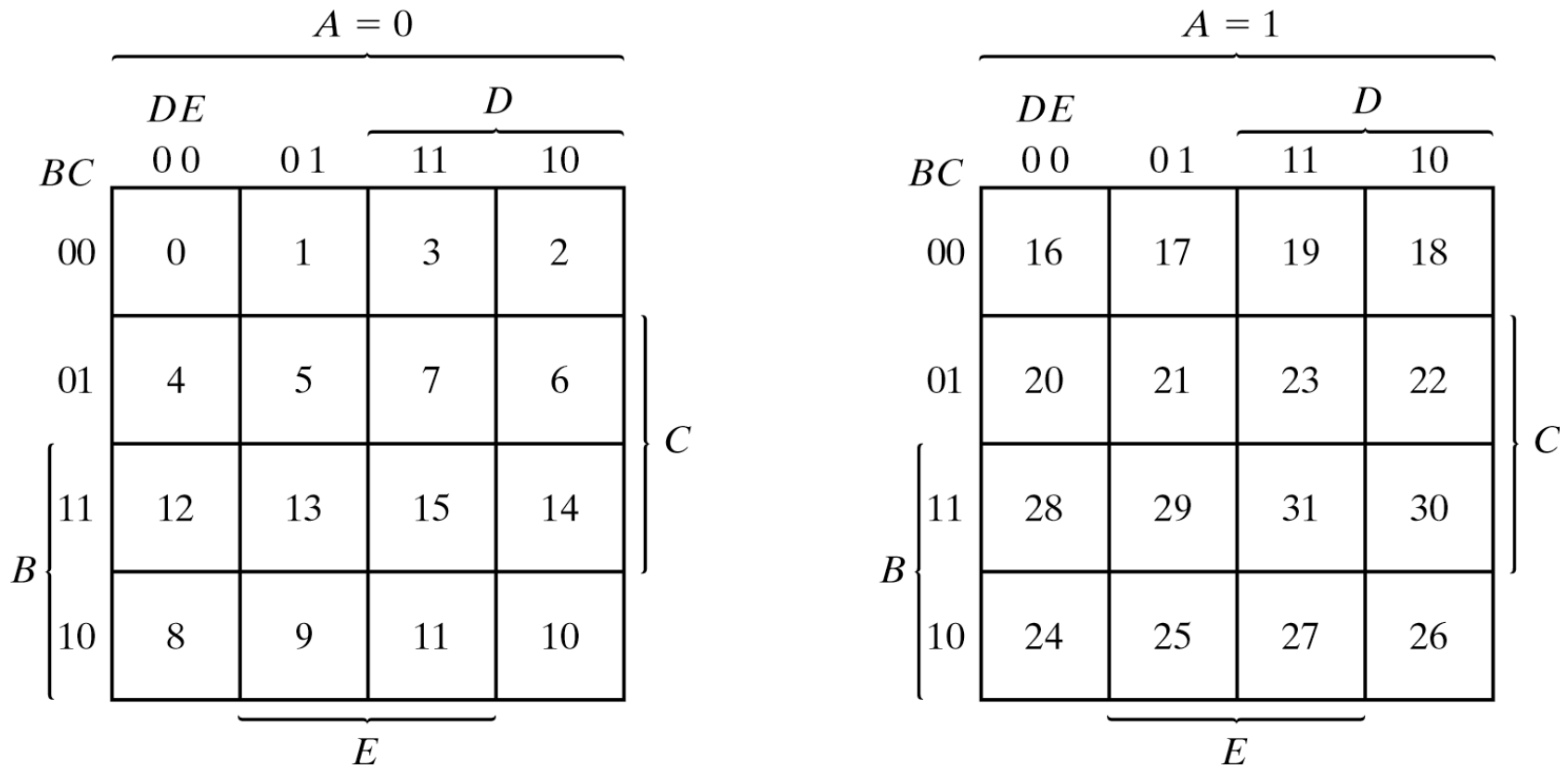


Figure 3.12 Five-variable Map

Example 3.7

Example 3.7: simplify $F = \Sigma(0, 2, 4, 6, 9, 13, 21, 23, 25, 29, 31)$

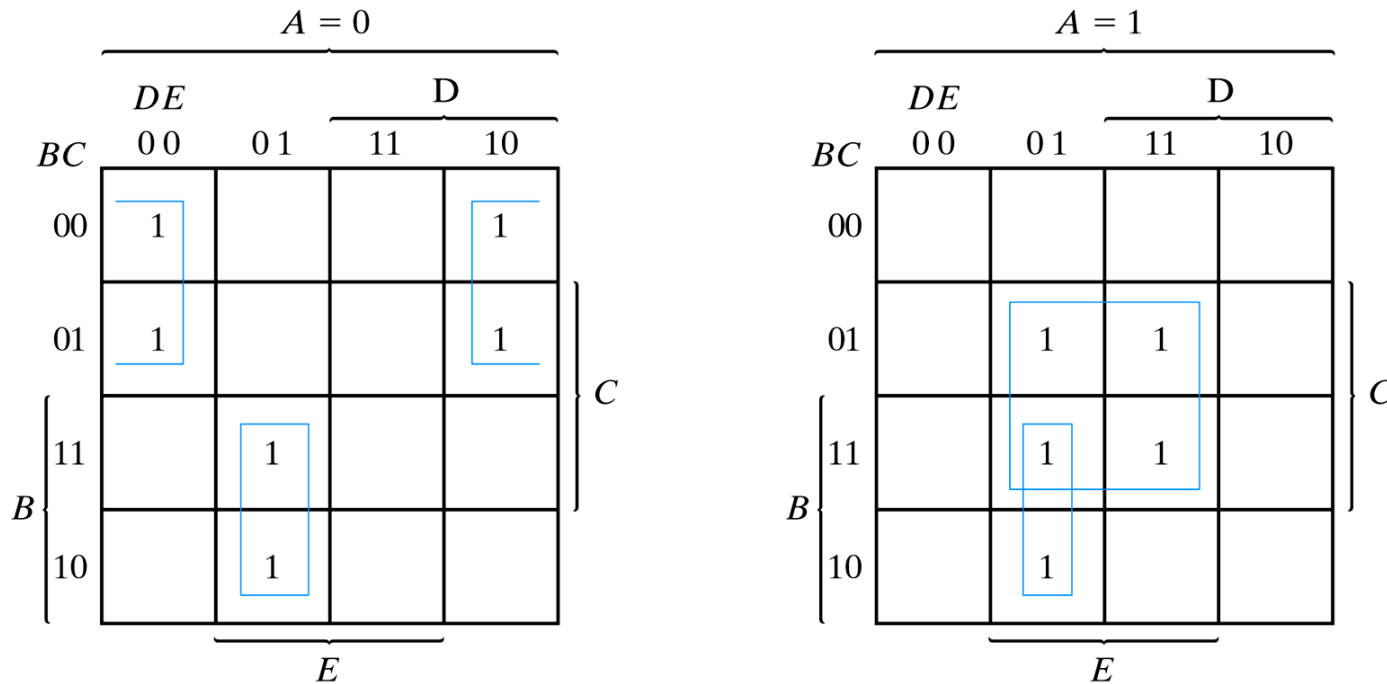


Fig. 3-13 Map for Example 3-7; $F = A'B'E' + BD'E + ACE$



$$F = A'B'E' + BD'E + ACE$$

3-5 Product of Sums Simplification

Approach #1

- ◆ Simplified F' in the form of sum of products
- ◆ Apply DeMorgan's theorem $F = (F')'$
- ◆ F' : sum of products $\rightarrow F$: product of sums


Approach #2: duality

- ◆ Combinations of maxterms (it was minterms)
- ◆ $M_0 M_1 = (A+B+C+D)(A+B+C+D)' = (A+B+C) + (DD)' = A+B+C$

AB \ CD	CD			
	00	01	11	10
00	M_0	M_1	M_3	M_2
01	M_4	M_5	M_7	M_6
11	M_{12}	M_{13}	M_{15}	M_{14}
10	M_8	M_9	M_{11}	M_{10}

Example 3.8

 - Example 3.8: simplify $F = \Sigma(0, 1, 2, 5, 8, 9, 10)$ into (a) sum-of-products form, and (b) product-of-sums form:




Note: $BC'D' + BCD' = BD'$

- $F(A, B, C, D) = \Sigma(0, 1, 2, 5, 8, 9, 10) = B'D' + B'C' + A'C'D$
- $F' = AB + CD + BD'$
 - » Apply DeMorgan's theorem;
 $F = (A' + B')(C' + D')(B' + D)$
 - » Or think in terms of maxterms

Figure 3.14 Map for Example 3.8, $F(A, B, C, D) = \Sigma(0, 1, 2, 5, 8, 9, 10) = B'D' + B'C' + A'C'D$

 
Example 3.8 (cont.)

Gate implementation of the function of Example 3.8



(a) $F = B'D' + B'C' + A'C'D$

Sum-of products form

 

(b) $F = (A' + B')(C' + D')(B' + D)$

Product-of sums form

Figure 3.15 Gate Implementation of the Function of Example 3.8

Sum-of-Minterm Procedure

■ Consider the function defined in Table 3.2.

◆ In sum-of-minterm:

$$F(x, y, z) = \sum (1, 3, 4, 6)$$

◆ In product-of-maxterm:

$$F(x, y, z) = \Pi(0, 2, 5, 7)$$

Table 3.2

Truth Table of Function F

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

Sum-of-Minterm Procedure

■ Consider the function defined in Table 3.2.

◆ Combine the 1's:

$$F(x, y, z) = x'z + xz'$$

◆ Combine the 0's :

$$F'(x, y, z) = xz + x'z'$$

◆ Taking the complement of F'

$$F(x, y, z) = (x' + z')(x + z)$$

 



Figure 3.16 Map for the function of Table 3.2

3-6 Don't-Care Conditions


- ▣ The value of a function is not specified for certain combinations of variables
 - ◆ BCD; 1010-1111: don't care
- ▣ The don't-care conditions can be utilized in logic minimization
 - ◆ Can be implemented as 0 or 1
- ▣ Example 3.9: simplify $F(w, x, y, z) = \Sigma(1, 3, 7, 11, 15)$ which has the don't-care conditions $d(w, x, y, z) = \Sigma(0, 2, 5)$.

 Example 3.9 (cont.)

- ◆ (a) $F = yz + w'x'$; there for $F = \Sigma(0, 1, 2, 3, 7, 11, 15)$
- ◆ (b) $F = yz + w'z$ there for $F = \Sigma(1, 3, 5, 7, 11, 15)$
- ◆ Either expression is acceptable



(a) $F = yz + w'x'$

 

(b) $F = yz + w'z$

Figure 3.17 Example with don't-care Conditions

Home Work (5)

Digital Design (4th)- Morris Mano-Page 116-
Problems:

3.2 d, e, f

3.4 e & f

3.7

3.12

3.15

3-7 NAND and NOR Implementation

- NAND and NOR gates are *easier* to fabricate with electronic components.
- Digital circuits are frequently *constructed* with NAND or NOR gates rather than with AND and OR gates.
- *rules and procedures* have been developed for the *conversion* from Boolean functions given in terms of AND, OR and NOT into equivalent NAND and NOR logic diagrams.

NAND Gate

- NAND gate is a universal gate
 - ◆ Can implement any digital system

 


Figure 3.18 Logic Operations with NAND Gates

NAND Gate

- Two graphic symbols for a NAND gate

 


Figure 3.19 Two Graphic Symbols for NAND Gate

Procedure with Two Levels NAND

- The procedure to implement Boolean function with two level NAND:
 - ◆ Simplified in the form of sum of products;
 - ◆ A NAND gate for each product term; the inputs to each NAND gate are the literals of the term (the first level);
 - ◆ A single NAND gate for the second sum term (the second level);
 - ◆ A term with a single literal requires an inverter in the first level.

Example 3.10

Example 3-10: implement $F(x, y, z) = \sum (1,2,3,4,5,7)$

$$F(x, y, z) = \sum (1,2,3,4,5,7) \longrightarrow F(x, y, z) = xy' + x'y + z$$

 


Figure 3.21 Solution to Example 3-10

Multilevel NAND Circuits

□ Boolean function implementation

◆ AND-OR logic \rightarrow NAND-NAND logic

» AND \rightarrow AND + inverter

» OR: inverter + OR = NAND

» For every **bubble** that is not compensated by another bubble along the same line, insert an inverter.



 


Figure 3.22 Implementing $F = A(CD + B) + BC'$

NAND Implementation

 

(a) AND-OR gates

 

(b) NAND gates

Figure 3.23 Implementing $F = (AB' + A'B)(C + D)$

NOR Implementation

- ▣ NOR function is the dual of NAND function.
- ▣ The NOR gate is also universal.



 


Figure 3.24 Logic Operation with NOR Gates

Two Graphic Symbols for a NOR Gate

 

(a) OR-invert

 

(b) Invert-AND

Figure 3.25 Two Graphic Symbols for NOR Gate

Example: $F = (A + B)(C + D)E$

 


Figure 3.26 Implementing $F = (A + B)(C + D)E$

Example

Example: Implement $F = (AB' + A'B)(C + D')$ with NOR gates

 


Figure 3.27 Implementing $F = (AB' + A'B)(C + D')$ with NOR gates

3-9 Exclusive-OR Function

■ Exclusive-OR (XOR) $x \oplus y = xy' + x'y$

■ Exclusive-NOR (XNOR)

◆ $(x \oplus y)' = xy + x'y'$

■ Some identities

◆ $x \oplus 0 = x$

◆ $x \oplus 1 = x'$

◆ $x \oplus x = 0$

◆ $x \oplus x' = 1$

◆ $x \oplus y' = (x \oplus y)'$

◆ $x' \oplus y = (x \oplus y)'$

■ Commutative and associative


◆ $A \oplus B = B \oplus A$

◆ $(A \oplus B) \oplus C = A \oplus (B \oplus C) = A \oplus B \oplus C$

 
3.9 Exclusive-OR Implementations

▣ Implementations

◆ $x \oplus y = xy' + x'y = (x' + y)x + (x' + y')y$



(a) With AND-OR-NOT gates

 

(b) With NAND gates

Figure 3.32 Exclusive-OR Implementations

Odd Function

- ◆ $A \oplus B \oplus C = (AB' + A'B)C' + (AB + A'B')C = AB'C' + A'BC' + ABC + A'B'C = \Sigma(1, 2, 4, 7)$
- ◆ XOR is a odd function \rightarrow an odd number of 1's, then $F = 1$.
- ◆ XNOR is a even function \rightarrow an even number of 1's, then $F = 1$.

BC		B			
		00	01	11	10
A	0	m_0	m_1 1	m_3	m_2 1
	1	m_4 1	m_5	m_7 1	m_6

(a) Odd function $F = A \oplus B \oplus C$


BC		B			
		00	01	11	10
A	0	m_0 1	m_1	m_3 1	m_2
	1	m_4	m_5 1	m_7	m_6 1

(b) Even function $F = (A \oplus B \oplus C)'$


Figure 3.33 Map for a Three-variable Exclusive-OR Function

XOR and XNOR

 ▣ Logic diagram of odd and even functions



(a) 3-input odd function

 


(b) 3-input even function

Figure 3.34 Logic Diagram of Odd and Even Functions


Parity Generation and Checking

■ Parity Generation and Checking

 - ◆ A parity bit: $P = x \oplus y \oplus z$
- ◆ Parity check: $C = x \oplus y \oplus z \oplus P$
 - » $C=1$: one bit error or an odd number of data bit error
 - » $C=0$: correct or an even number of data bit error



(a) 3-bit even parity generator

 

(b) 4-bit even parity checker

Figure 3.36 Logic Diagram of a Parity Generator and Checker

Parity Generation and Checking

Table 3.4

Even-Parity-Generator Truth Table

Three-Bit Message			Parity Bit
<i>x</i>	<i>y</i>	<i>z</i>	<i>P</i>
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Parity Generation and Checking

Table 3.5
Even-Parity-Checker Truth Table

Four Bits Received				Parity Error Check
<i>x</i>	<i>y</i>	<i>z</i>	<i>P</i>	<i>C</i>
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

Home Work (6)

Digital Design (4th)- Morris Mano-Page 116-
Problems:

3.16 b, c,

3. 17

3.20

3.21

3.23

تم بحمد الله