
Digital Logic Design


Chapter 4

Combinational Logic

Combinational Circuits

- Output is function of input only (present combination of inputs).

i.e. no feedback

 


When **input** changes, **output** may change (after a delay)

Combinational Circuits


□ Analysis

 - ◆ Given a circuit, find out its *function*
- ◆ Function may be expressed as:
 - » Boolean function
 - » Truth table




□ Design

 - ◆ Given a desired function, determine its *circuit*
- ◆ Function may be expressed as:
 - » Boolean function
 - » Truth table



Analysis Procedure

■ Boolean Expression Approach

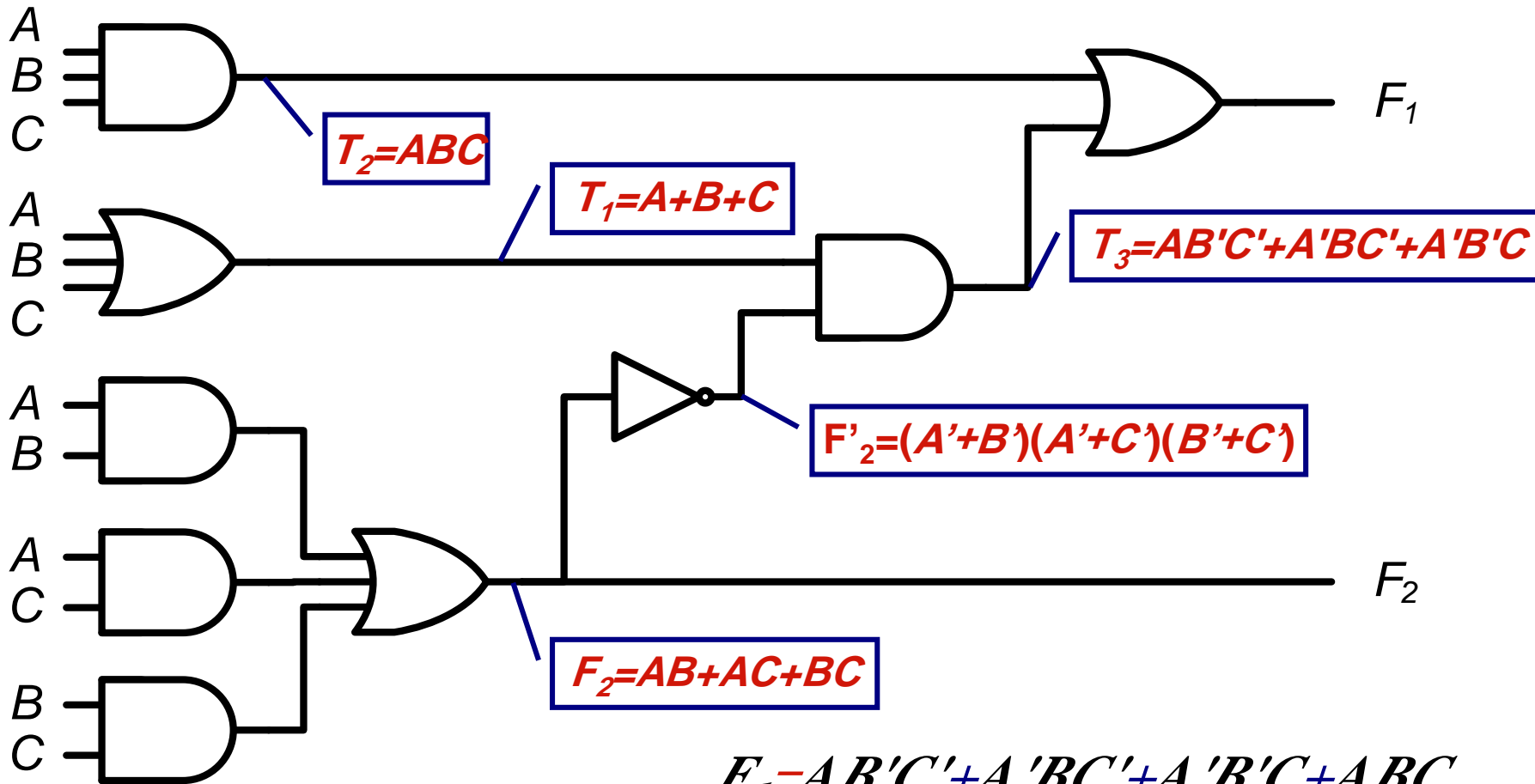


$$F_1 = AB'C' + A'BC' + A'B'C + ABC$$

$$F_2 = AB + AC + BC$$

Analysis Procedure


Truth Table Approach

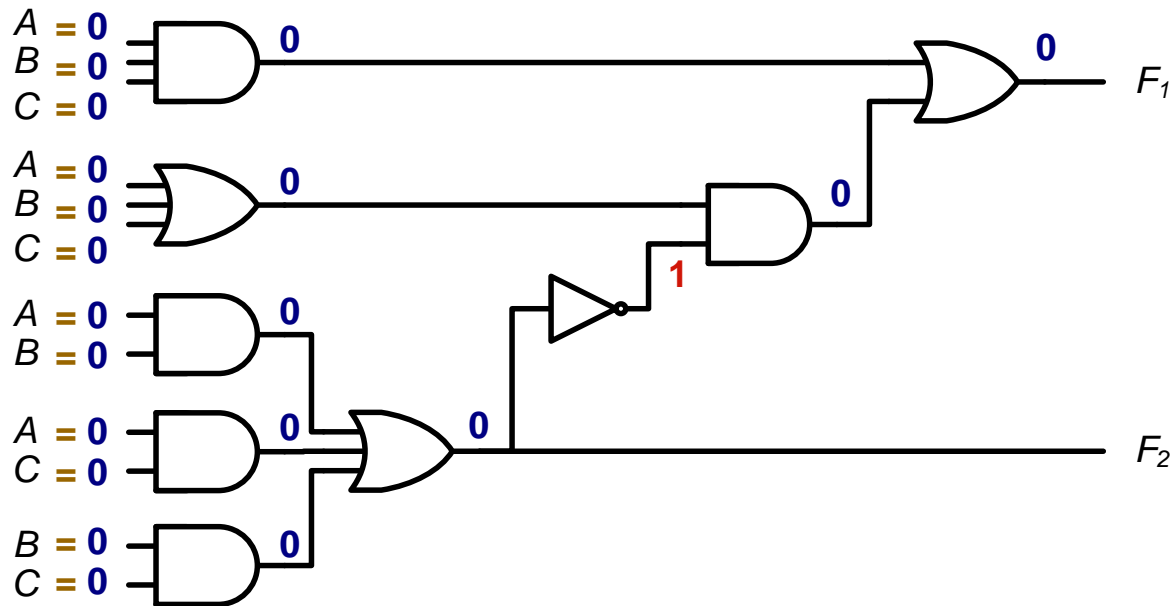

| <i>A</i> | <i>B</i> | <i>C</i> | <i>F₁</i> | <i>F₂</i> |
|----------|----------|----------|----------------------|----------------------|
| 0 | 0 | 0 | 0 | 0 |
| | | | | |
| | | | | |
| | | | | |
| | | | | |
| | | | | |
| | | | | |
| | | | | |

Analysis Procedure


Truth Table Approach

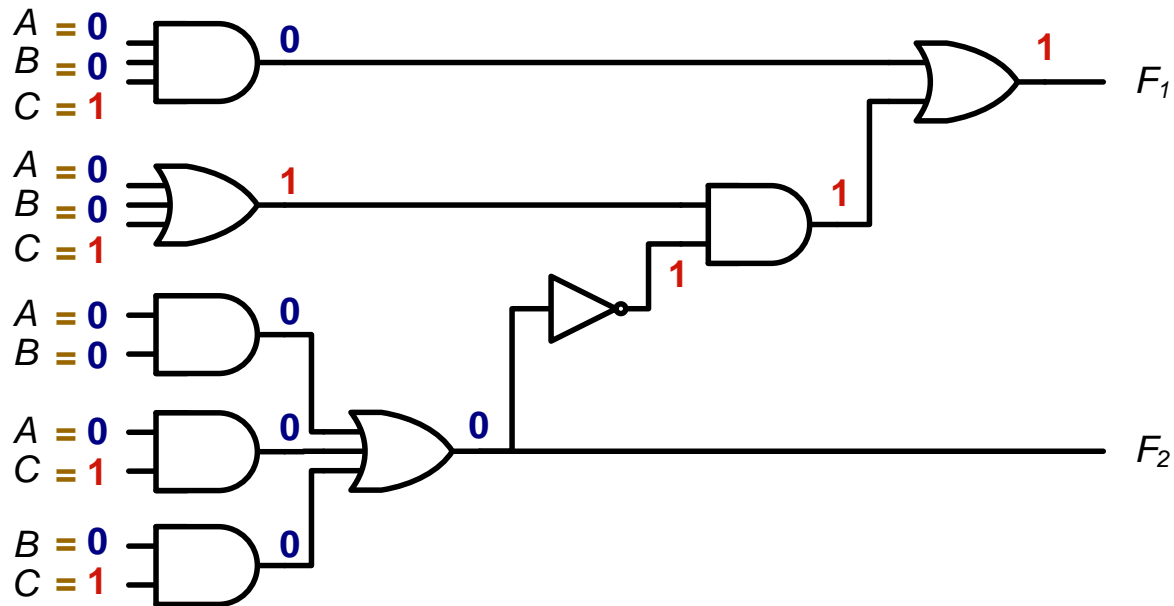

| <i>A</i> | <i>B</i> | <i>C</i> | <i>F₁</i> | <i>F₂</i> |
|----------|----------|----------|----------------------|----------------------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| | | | | |
| | | | | |
| | | | | |
| | | | | |
| | | | | |
| | | | | |

Analysis Procedure


Truth Table Approach

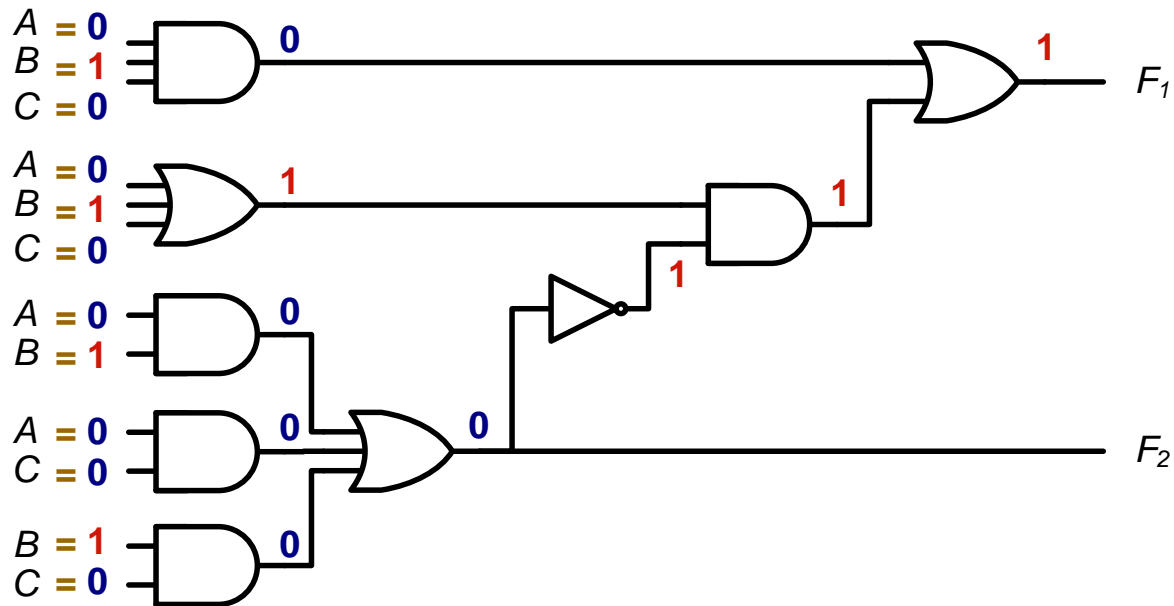

| A | B | C | F_1 | F_2 |
|-----|-----|-----|-------|-------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| | | | | |
| | | | | |
| | | | | |
| | | | | |
| | | | | |

Analysis Procedure


Truth Table Approach

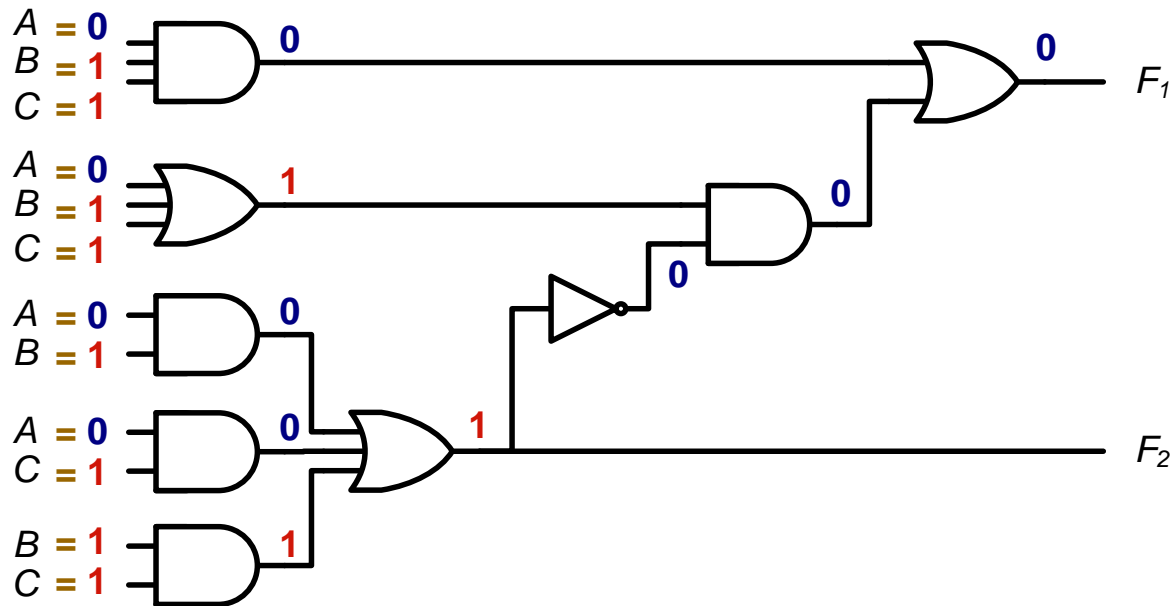

| A | B | C | F_1 | F_2 |
|---|---|---|-------|-------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| | | | | |
| | | | | |
| | | | | |
| | | | | |

Analysis Procedure


Truth Table Approach

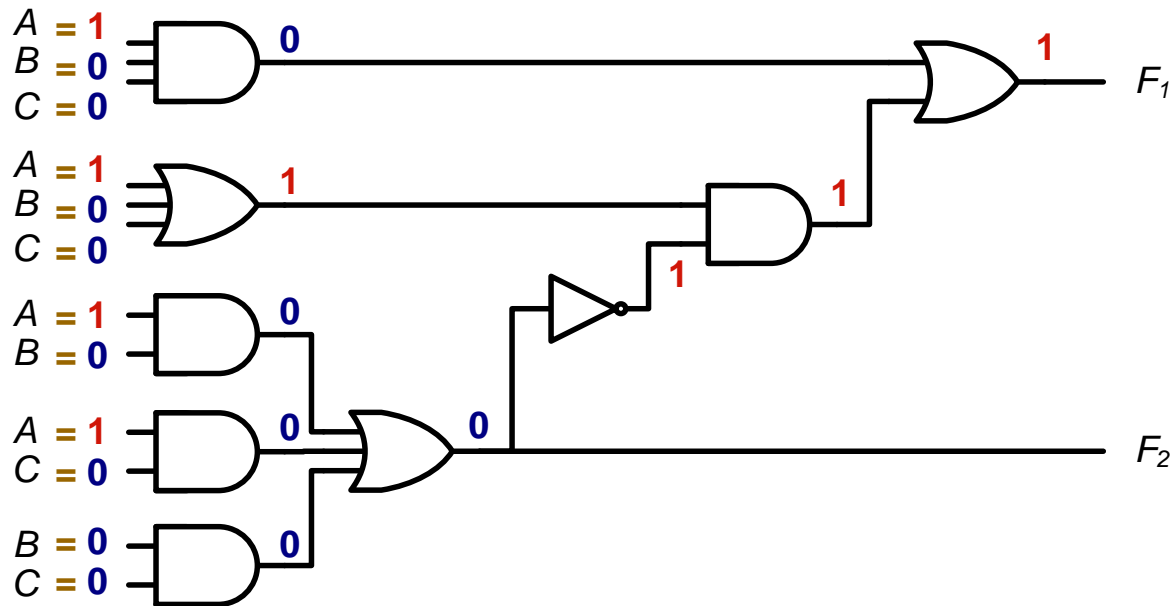

| A | B | C | F_1 | F_2 |
|-----|-----|-----|-------|-------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| | | | | |
| | | | | |
| | | | | |

Analysis Procedure


Truth Table Approach

 

| A | B | C | F_1 | F_2 |
|-----|-----|-----|-------|-------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| | | | | |
| | | | | |

Analysis Procedure


Truth Table Approach

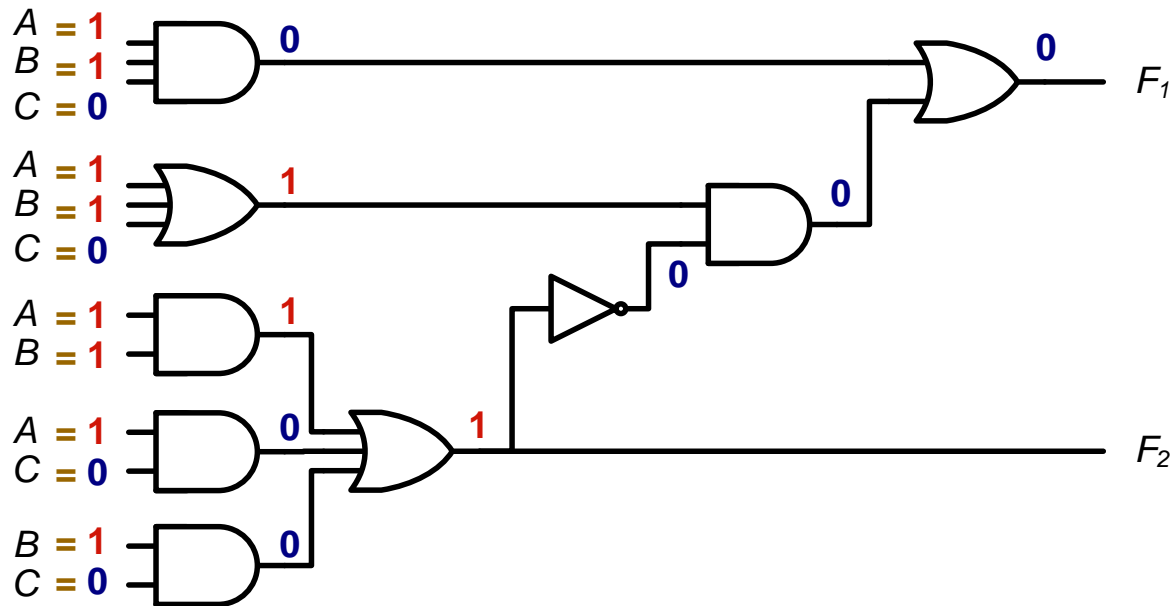

| A | B | C | F_1 | F_2 |
|-----|-----|-----|-------|-------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| | | | | |

Analysis Procedure

Truth Table Approach

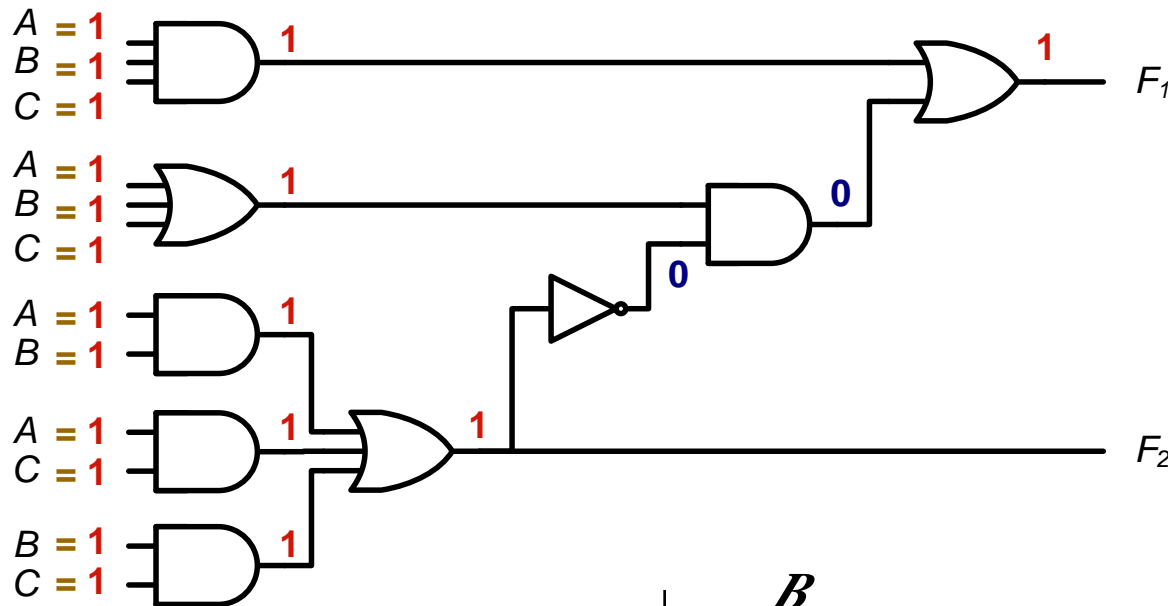

| A | B | C | F_1 | F_2 |
|-----|-----|-----|-------|-------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

| | | | | |
|-----|-----|---|---|---|
| | B | | | |
| | 0 | 1 | 0 | 1 |
| A | 1 | 0 | 1 | 0 |
| | C | | | |

| | | | | |
|-----|-----|---|---|---|
| | B | | | |
| | 0 | 0 | 1 | 0 |
| A | 0 | 1 | 1 | 1 |
| | C | | | |

$$F_1 = AB'C' + A'BC' + A'B'C + ABC$$

$$F_2 = AB + AC + BC$$


Design Procedure

□ Given a problem statement:

- ◆ Determine the number of *inputs* and *outputs*
- ◆ Derive the truth table
- ◆ Simplify the Boolean expression for each output
- ◆ Produce the required circuit

 Example:


Design a circuit to convert a “BCD” code to “Excess 3” code




Design Procedure

BCD-to-Excess 3 Converter


| <i>A B C D</i> | <i>w x y z</i> |
|----------------|----------------|
| 0 0 0 0 | 0 0 1 1 |
| 0 0 0 1 | 0 1 0 0 |
| 0 0 1 0 | 0 1 0 1 |
| 0 0 1 1 | 0 1 1 0 |
| 0 1 0 0 | 0 1 1 1 |
| 0 1 0 1 | 1 0 0 0 |
| 0 1 1 0 | 1 0 0 1 |
| 0 1 1 1 | 1 0 1 0 |
| 1 0 0 0 | 1 0 1 1 |
| 1 0 0 1 | 1 1 0 0 |
| 1 0 1 0 | x x x x |
| 1 0 1 1 | x x x x |
| 1 1 0 0 | x x x x |
| 1 1 0 1 | x x x x |
| 1 1 1 0 | x x x x |
| 1 1 1 1 | x x x x |

 


$$w = A + BC + BD$$

 

$$x = B'C + B'D + BC'D'$$

 

$$y = C'D' + CD$$

 


$$z = D'$$

Design Procedure

BCD-to-Excess 3 Converter

| <i>A B C D</i> | <i>w x y z</i> |
|----------------|----------------|
| 0 0 0 0 | 0 0 1 1 |
| 0 0 0 1 | 0 1 0 0 |
| 0 0 1 0 | 0 1 0 1 |
| 0 0 1 1 | 0 1 1 0 |
| 0 1 0 0 | 0 1 1 1 |
| 0 1 0 1 | 1 0 0 0 |
| 0 1 1 0 | 1 0 0 1 |
| 0 1 1 1 | 1 0 1 0 |
| 1 0 0 0 | 1 0 1 1 |
| 1 0 0 1 | 1 1 0 0 |
| 1 0 1 0 | x x x x |
| 1 0 1 1 | x x x x |
| 1 1 0 0 | x x x x |
| 1 1 0 1 | x x x x |
| 1 1 1 0 | x x x x |
| 1 1 1 1 | x x x x |

 

$$w = A + B(C + D)$$




$$y = (C + D)' + CD$$

$$x = B'(C + D) + B(C + D)'$$

$$z = D'$$

Seven-Segment Decoder

| <i>w x y z</i> | <i>a b c d e f g</i> |
|----------------|----------------------|
| 0 0 0 0 | 1 1 1 1 1 1 0 |
| 0 0 0 1 | 0 1 1 0 0 0 0 |
| 0 0 1 0 | 1 1 0 1 1 0 1 |
| 0 0 1 1 | 1 1 1 1 0 0 1 |
| 0 1 0 0 | 0 1 1 0 0 1 1 |
| 0 1 0 1 | 1 0 1 1 0 1 1 |
| 0 1 1 0 | 1 0 1 1 1 1 1 |
| 0 1 1 1 | 1 1 1 0 0 0 0 |
| 1 0 0 0 | 1 1 1 1 1 1 1 |
| 1 0 0 1 | 1 1 1 1 0 1 1 |
| 1 0 1 0 | x x x x x x x |
| 1 0 1 1 | x x x x x x x |
| 1 1 0 0 | x x x x x x x |
| 1 1 0 1 | x x x x x x x |
| 1 1 1 0 | x x x x x x x |
| 1 1 1 1 | x x x x x x x |

   

$$a = w + y + xz + x'z'$$

$$b = \dots$$

$$c = \dots$$

$$d = \dots$$




Binary Adder


■ Half Adder

- ◆ Adds 1-bit plus 1-bit
- ◆ Produces Sum and Carry
 
$$\begin{array}{r} x \\ + y \\ \hline C \quad S \end{array}$$



| $x \ y$ | $S \ C$ |
|---------|---------|
| $0 \ 0$ | $0 \ 0$ |
| $0 \ 1$ | $1 \ 0$ |
| $1 \ 0$ | $1 \ 0$ |
| $1 \ 1$ | $0 \ 1$ |

 

Binary Adder

Full Adder

- ◆ Adds 1-bit plus 1-bit plus 1-bit (carry from the previous position)
- ◆ Produces Sum and Carry

| x | y | z | S | C |
|-----|-----|-----|-----|-----|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

| | y | | | |
|-----|-----|---|---|---|
| | 0 | 1 | 0 | 1 |
| x | 1 | 0 | 1 | 0 |

z


$$S = xy'z' + x'y'z + x'yz + xyz = x \oplus y \oplus z$$

| | y | | | |
|-----|-----|---|---|---|
| | 0 | 0 | 1 | 0 |
| x | 0 | 1 | 1 | 1 |

z

$$C = xy + xz + yz$$
 
$$\begin{array}{r} x \\ + y \\ + z \\ \hline C \quad S \end{array}$$





Binary Adder

Full Adder



$$S = xy'z' + x'y'z + x'yz + xyz = x \oplus y \oplus z$$

$$C = xy + xz + yz$$

 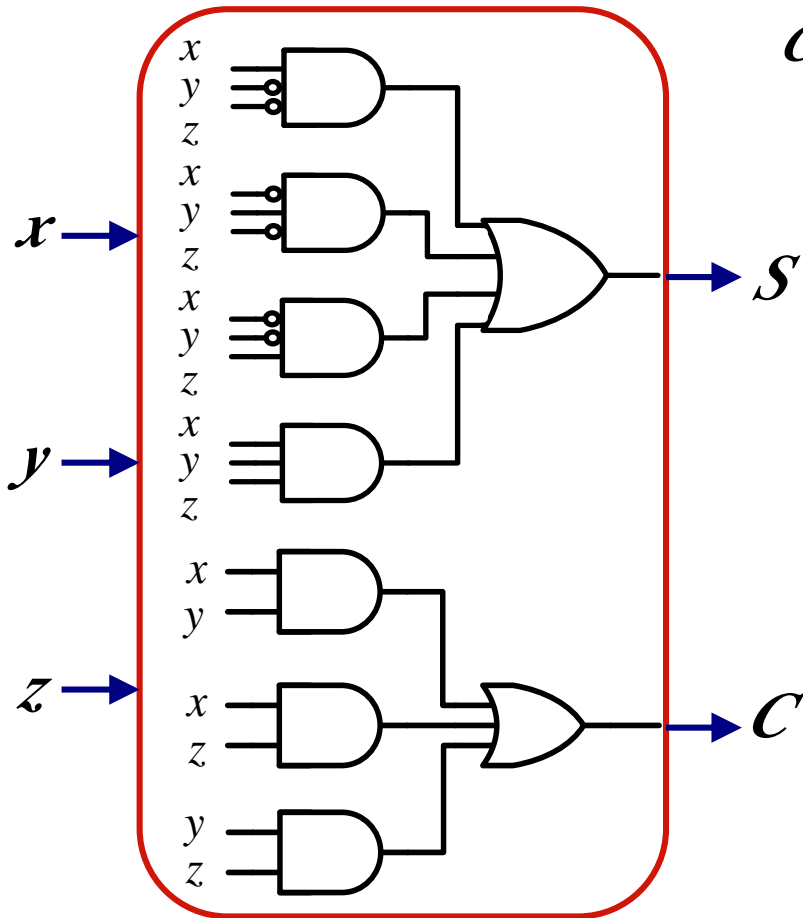


Binary Adder

■ Full Adder = Two half adder + OR gate

  


Binary Adder

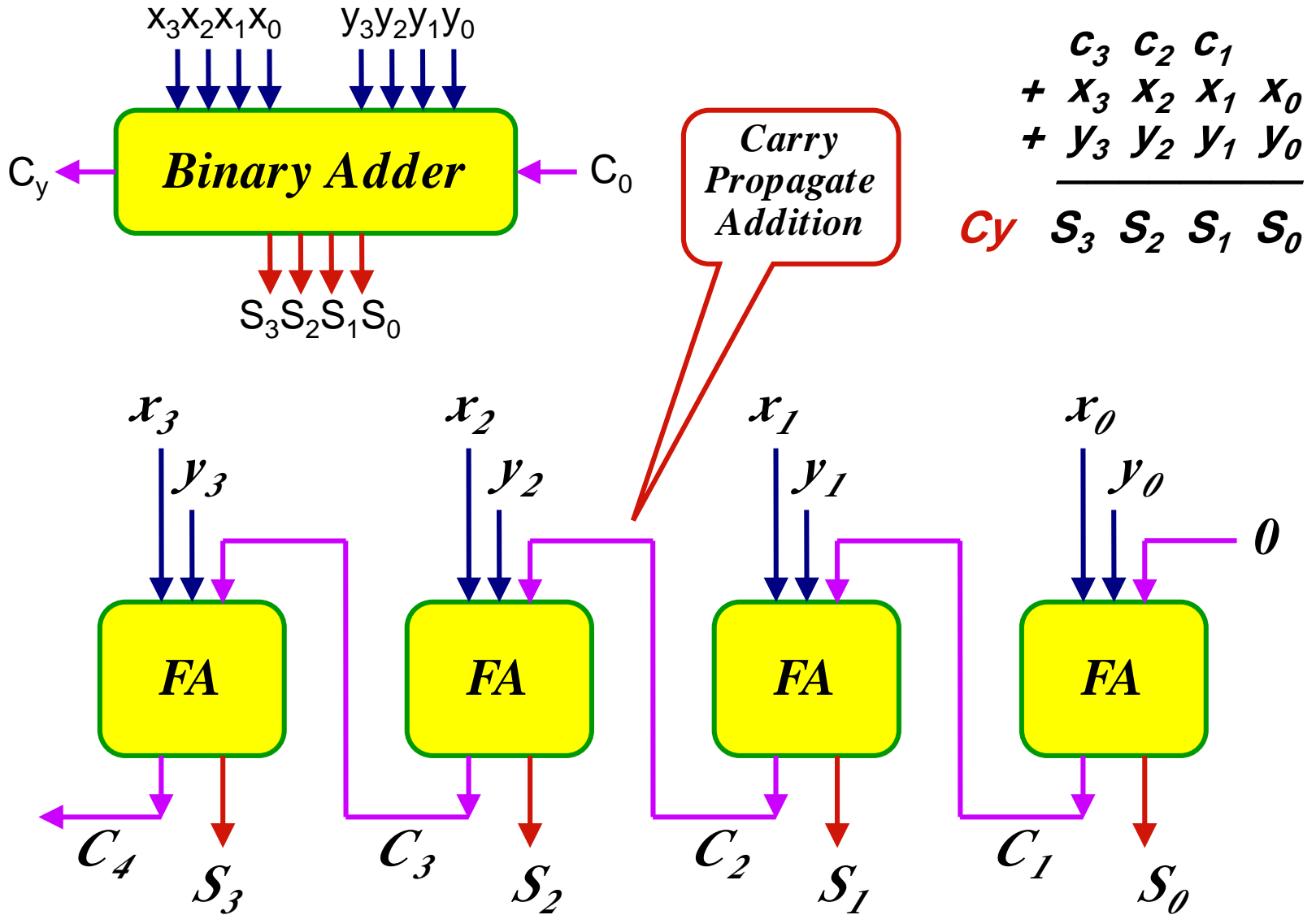

Binary Adder


□ Carry Propagate Adders

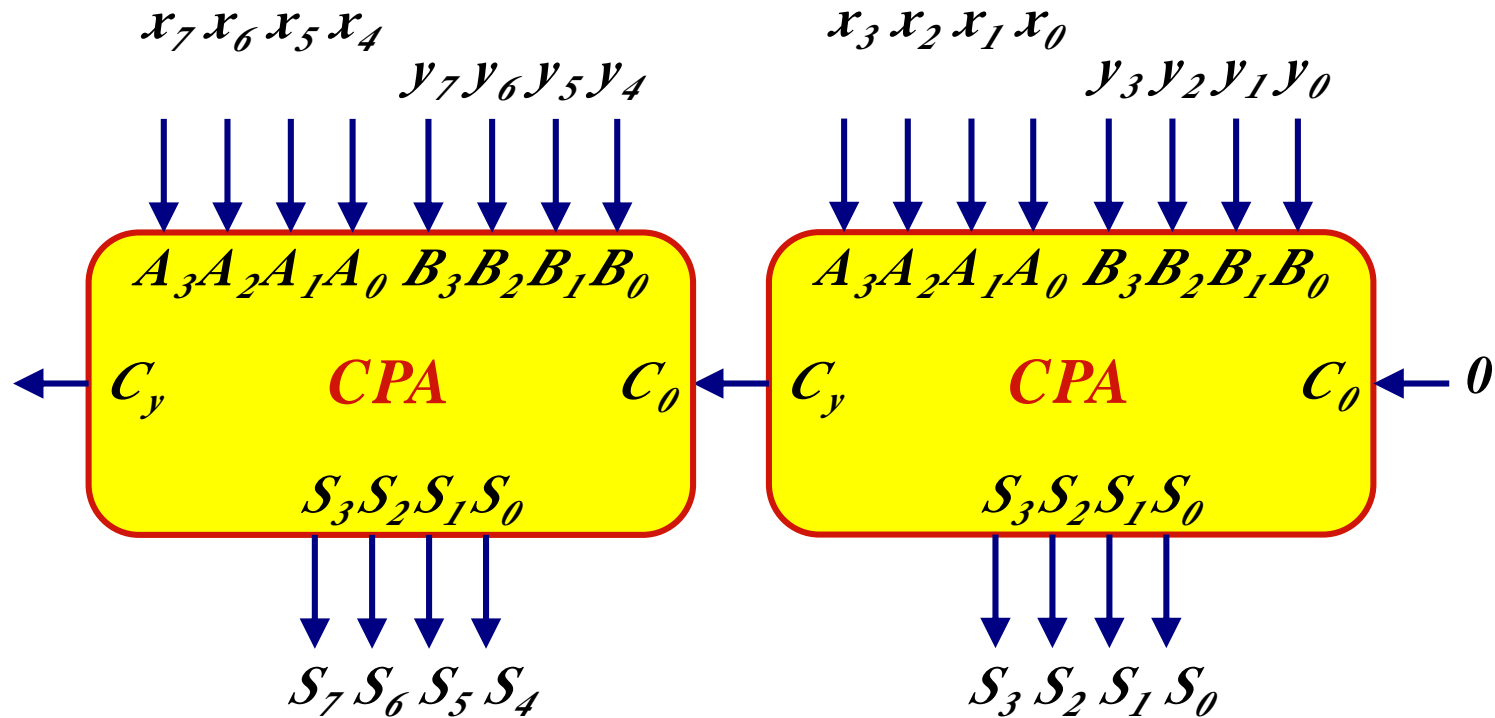

Binary Subtractor

▣ Use 2's complement with binary adder

◆ $x - y = x + (-y) = x + y' + 1$

 


Binary Adder/Subtractor

▣ M : Control Signal (Mode)


◆ $M=0 \rightarrow F = x + y$

◆ $M=1 \rightarrow F = x - y$

 


Carry and Overflow

■ Unsigned Binary Numbers

 

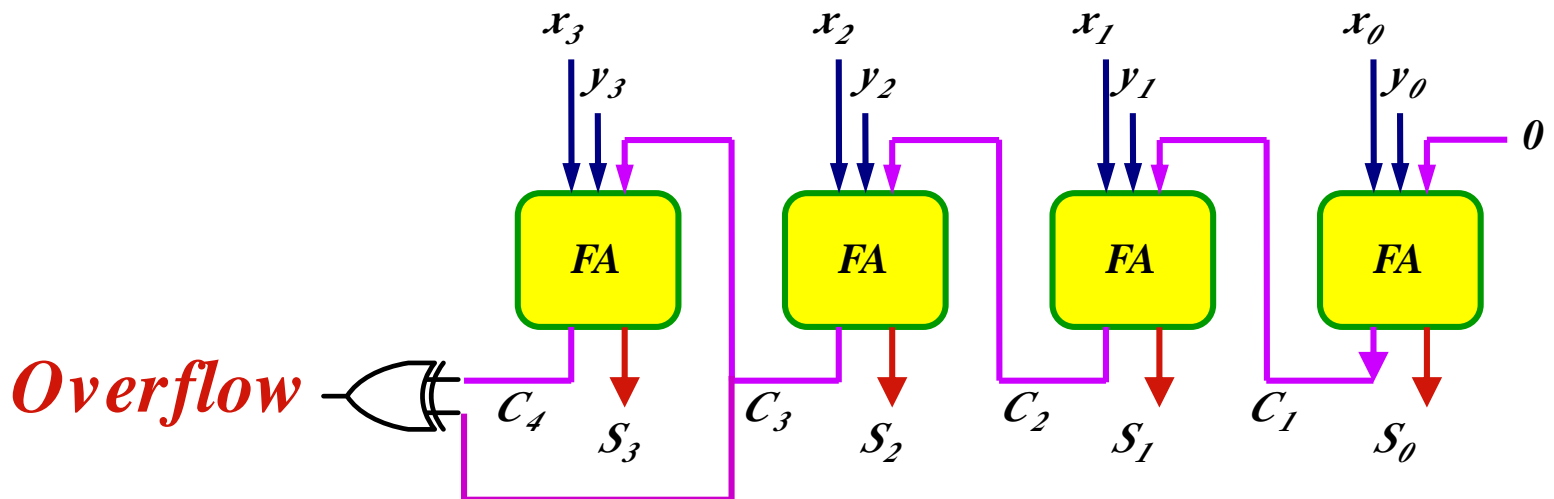■ Signed Numbers: 2's Complement Numbers (overflow may occur if the two numbers added are *both* positive or negative.)



BCD Adder

- 4-bits plus 4-bits
- Operands and Result: 0 to 9

$$\begin{array}{r}
 + x_3 x_2 x_1 x_0 \\
 + y_3 y_2 y_1 y_0 \\
 \hline
 \end{array}$$

Cy $s_3 s_2 s_1 s_0$

| $X+Y$ | $x_3 x_2 x_1 x_0$ | $y_3 y_2 y_1 y_0$ | <i>Sum</i> | <i>Cy</i> | $s_3 s_2 s_1 s_0$ |
|-------|-------------------|-------------------|------------|-----------|-------------------|
| $0+0$ | 0 0 0 0 | 0 0 0 0 | = 0 | 0 | 0 0 0 0 |
| $0+1$ | 0 0 0 0 | 0 0 0 1 | = 1 | 0 | 0 0 0 1 |
| $0+2$ | 0 0 0 0 | 0 0 1 0 | = 2 | 0 | 0 0 1 0 |
| | | | | | |
| $0+9$ | 0 0 0 0 | 1 0 0 1 | = 9 | 0 | 1 0 0 1 |
| $1+0$ | 0 0 0 1 | 0 0 0 0 | = 1 | 0 | 0 0 0 1 |
| $1+1$ | 0 0 0 1 | 0 0 0 1 | = 2 | 0 | 0 0 1 0 |
| | | | | | |
| $1+8$ | 0 0 0 1 | 1 0 0 0 | = 9 | 0 | 1 0 0 1 |
| $1+9$ | 0 0 0 1 | 1 0 0 1 | = A | 0 | 1 0 1 0 |
| $2+0$ | 0 0 1 0 | 0 0 0 0 | = 2 | 0 | 0 0 1 0 |
| | | | | | |
| $9+9$ | 1 0 0 1 | 1 0 0 1 | = 18 | 1 | 0 0 1 0 |

Invalid Code

Wrong BCD Value

0001 1000

BCD Adder

| $X+Y$ | $x_3x_2x_1x_0$ | $y_3y_2y_1y_0$ | Sum | Cy | $S_3S_2S_1S_0$ | $Required\ BCD\ Output$ | $Value$ |
|-------|----------------|----------------|-------|------|----------------|-------------------------|---------|
| $9+0$ | 1 0 0 1 | 0 0 0 0 | = 9 | 0 | 1 0 0 1 | 0 0 0 0 1 0 0 1 | = 9 |
| $9+1$ | 1 0 0 1 | 0 0 0 1 | = 10 | 0 | 1 0 1 0 | 0 0 0 1 0 0 0 0 | = 16 ✕ |
| $9+2$ | 1 0 0 1 | 0 0 1 0 | = 11 | 0 | 1 0 1 1 | 0 0 0 1 0 0 0 1 | = 17 ✕ |
| $9+3$ | 1 0 0 1 | 0 0 1 1 | = 12 | 0 | 1 1 0 0 | 0 0 0 1 0 0 1 0 | = 18 ✕ |
| $9+4$ | 1 0 0 1 | 0 1 0 0 | = 13 | 0 | 1 1 0 1 | 0 0 0 1 0 0 1 1 | = 19 ✕ |
| $9+5$ | 1 0 0 1 | 0 1 0 1 | = 14 | 0 | 1 1 1 0 | 0 0 0 1 0 1 0 0 | = 20 ✕ |
| $9+6$ | 1 0 0 1 | 0 1 1 0 | = 15 | 0 | 1 1 1 1 | 0 0 0 1 0 1 0 1 | = 21 ✕ |
| $9+7$ | 1 0 0 1 | 0 1 1 1 | = 16 | 1 | 0 0 0 0 | 0 0 0 1 0 1 1 0 | = 22 ✕ |
| $9+8$ | 1 0 0 1 | 1 0 0 0 | = 17 | 1 | 0 0 0 1 | 0 0 0 1 0 1 1 1 | = 23 ✕ |
| $9+9$ | 1 0 0 1 | 1 0 0 1 | = 18 | 1 | 0 0 1 0 | 0 0 0 1 1 0 0 0 | = 24 ✕ |


+ 6

BCD Adder

▣ Correct Binary Adder's Output (+6)

- ◆ If the result is between 'A' and 'F'
- ◆ If $C_y = 1$ (result greater than 'F')


| $S_3 S_2 S_1 S_0$ | <i>Err</i> |
|-------------------|------------|
| 0 0 0 0 | 0 |
| 1 0 0 0 | 0 |
| 1 0 0 1 | 0 |
| 1 0 1 0 | 1 |
| 1 0 1 1 | 1 |
| 1 1 0 0 | 1 |
| 1 1 0 1 | 1 |
| 1 1 1 0 | 1 |
| 1 1 1 1 | 1 |

 

$$Err = S_3 S_2 + S_3 S_1 + C_y$$

BCD Adder

$$Err = S_3 S_2 + S_3 S_1 + C_y$$

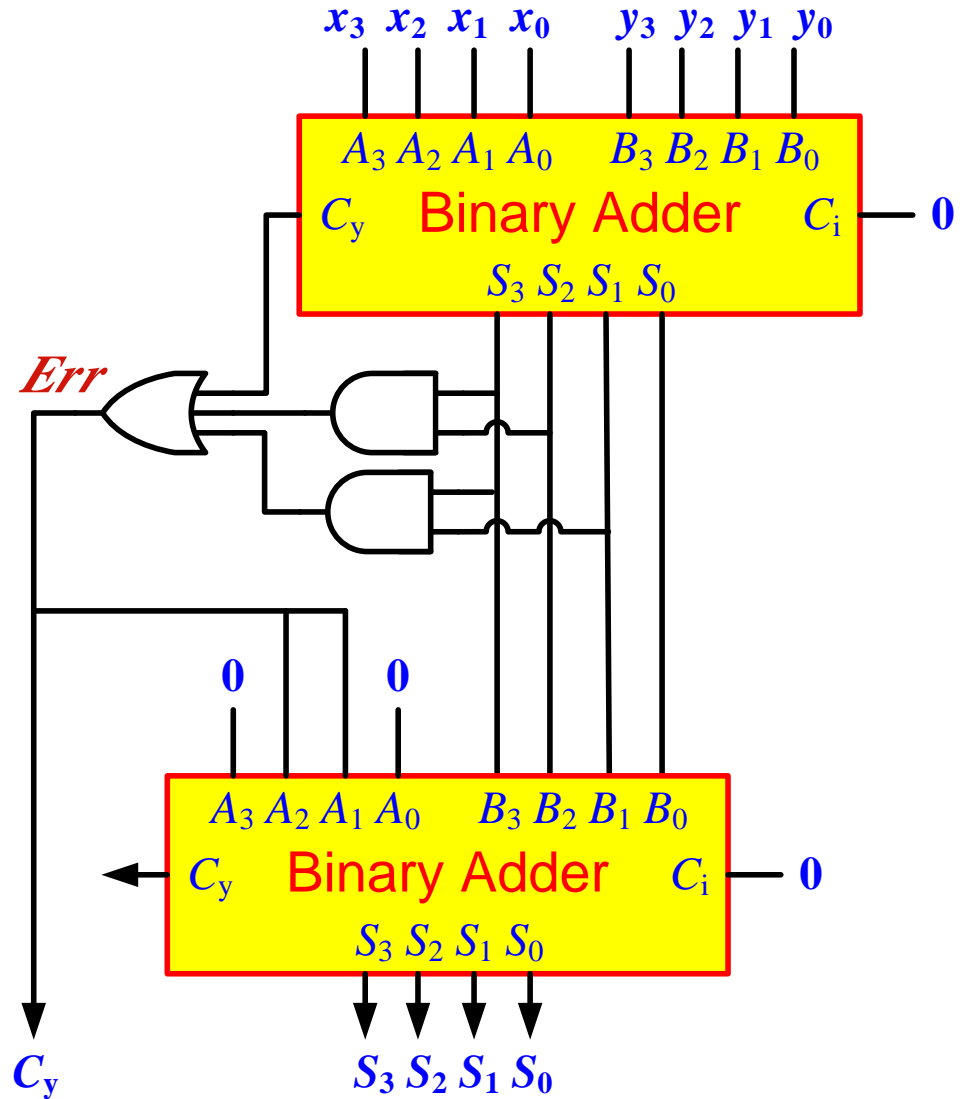

Home Work (7)

Digital Design (**4th**)- Morris Mano-Page **175**

-Problems:

4.4

4.5

4.6 (a)

4.7 (a)

4. 10

4.12

4.22

Magnitude Comparator

▣ Compare 4-bit number to 4-bit number

◆ 3 Outputs: $<$, $=$, $>$

$$x_3 = \bar{A}_3 \bar{B}_3 + A_3 B_3$$

$$x_2 = \bar{A}_2 \bar{B}_2 + A_2 B_2$$


$$x_1 = \bar{A}_1 \bar{B}_1 + A_1 B_1$$

$$x_0 = \bar{A}_0 \bar{B}_0 + A_0 B_0$$

$$(A = B) = x_3 x_2 x_1 x_0$$

$$(A > B) = A_3 \bar{B}_3 + x_3 A_2 \bar{B}_2 + x_3 x_2 A_1 \bar{B}_1 + x_3 x_2 x_1 A_0 \bar{B}_0$$
 
$$(A < B) = \bar{A}_3 B_3 + x_3 \bar{A}_2 B_2 + x_3 x_2 \bar{A}_1 B_1 + x_3 x_2 x_1 \bar{A}_0 B_0$$



Magnitude Comparator


 


Fig 4.17 : Four-bit magnitude Comparator

Magnitude Comparator


- Expandable to more number of bits

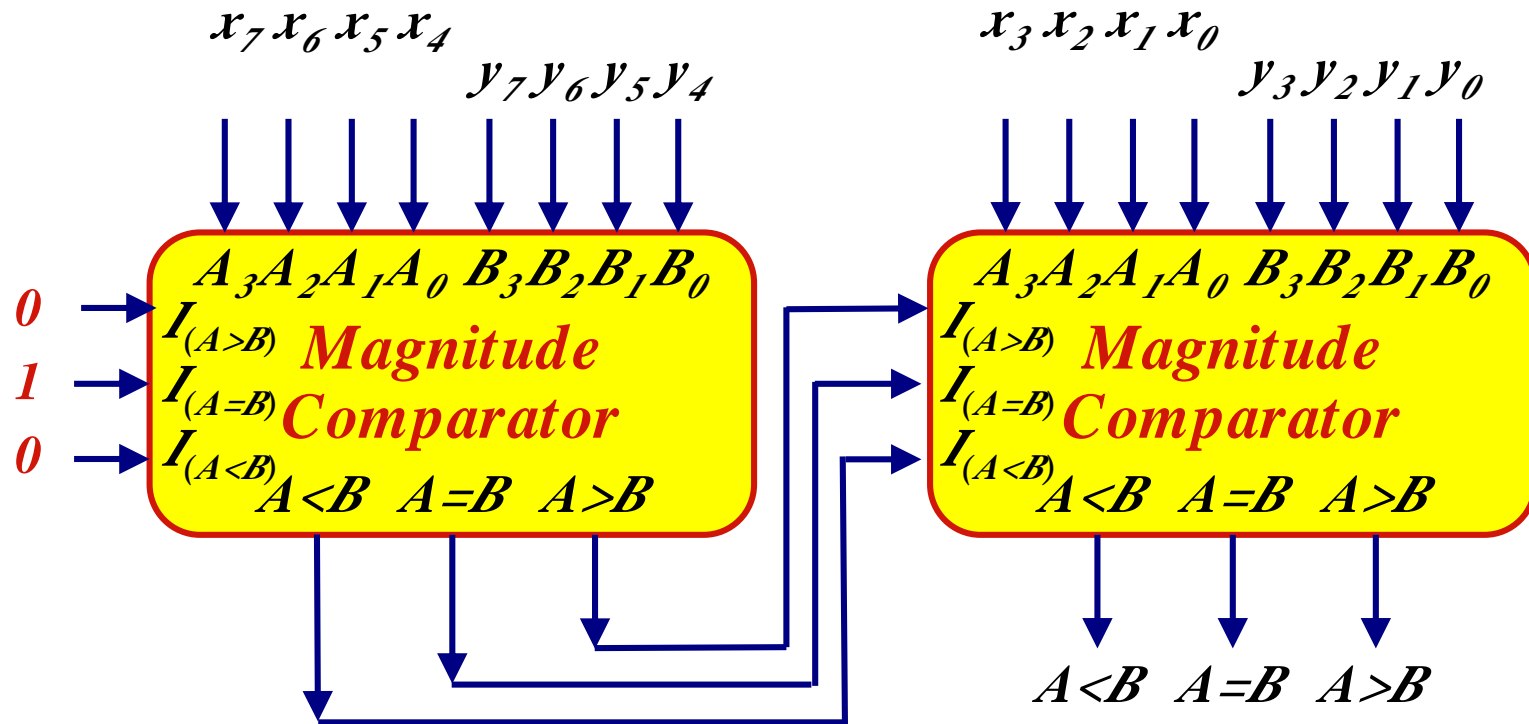

Decoders


- Extract “*Information*” from the code
- Binary Decoder
 - Example: 2-bit Binary Number

*Only **one** lamp will turn on*

 


Decoders

2-to-4 Line Decoder

 

| I_1 | I_0 | Y_3 | Y_2 | Y_1 | Y_0 |
|-------|-------|-------|-------|-------|-------|
| 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 0 | 1 | 0 | 0 |
| 1 | 1 | 1 | 0 | 0 | 0 |

 

$$Y_3 = I_1 I_0$$



$$Y_1 = \bar{I}_1 I_0$$

$$Y_2 = I_1 \bar{I}_0$$

$$Y_0 = \bar{I}_1 \bar{I}_0$$


Decoders

3-to-8 Line Decoder

  


Decoders

 - “*Enable*” input used to control the circuit operation




| E | I_1 I_0 | Y_3 Y_2 Y_1 Y_0 |
|-----|-------------|-------------------------|
| 0 | x x | 0 0 0 0 |
| 1 | 0 0 | 0 0 0 1 |
| 1 | 0 1 | 0 0 1 0 |
| 1 | 1 0 | 0 1 0 0 |
| 1 | 1 1 | 1 0 0 0 |

 

Decoders

Expansion

| $I_2 I_1 I_0$ | $Y_7 Y_6 Y_5 Y_4 Y_3 Y_2 Y_1 Y_0$ |
|---------------|-----------------------------------|
| 0 0 0 | 0 0 0 0 0 0 0 1 |
| 0 0 1 | 0 0 0 0 0 0 1 0 |
| 0 1 0 | 0 0 0 0 0 1 0 0 |
| 0 1 1 | 0 0 0 0 1 0 0 0 |
| 1 0 0 | 0 0 0 1 0 0 0 0 |
| 1 0 1 | 0 0 1 0 0 0 0 0 |
| 1 1 0 | 0 1 0 0 0 0 0 0 |
| 1 1 1 | 1 0 0 0 0 0 0 0 |



 


Decoders

■ Active-High / Active-Low

| I_1 | I_0 | Y_3 | Y_2 | Y_1 | Y_0 |
|-------|-------|-------|-------|-------|-------|
| 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 0 | 1 | 0 | 0 |
| 1 | 1 | 1 | 0 | 0 | 0 |

| I_1 | I_0 | Y_3 | Y_2 | Y_1 | Y_0 |
|-------|-------|-------|-------|-------|-------|
| 0 | 0 | 1 | 1 | 1 | 0 |
| 0 | 1 | 1 | 1 | 0 | 1 |
| 1 | 0 | 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 | 1 | 1 |

   

Uses NAND instead of AND


Implementation Using Decoders

- Each output is a minterm ($x'y'z' = Y_0$)
- All minterms are produced
- To implement a Boolean function sum the required minterms.

◆ Example: Full Adder


» $S(x, y, z) = \sum(1, 2, 4, 7)$

» $C(x, y, z) = \sum(3, 5, 6, 7)$

 

Encoders

 - Put “*Information*” into code
- Binary Encoder
 - Example: 4-to-2 Binary Encoder



*Only **one** switch should be activated at a time*

| x_3 | x_2 | x_1 | x_0 | y_1 | y_0 |
|-------|-------|-------|-------|-------|-------|
| 0 | 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 | 1 |

If **two** inputs are active simultaneously, the output produces an **undefined** combination

Encoders



■ Eight inputs Encoder (8-to-3)

| I_7 | I_6 | I_5 | I_4 | I_3 | I_2 | I_1 | I_0 | Y_2 | Y_1 | Y_0 |
|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 1 | 1 |

$$Y_2 = I_7 + I_6 + I_5 + I_4$$

$$Y_1 = I_7 + I_6 + I_3 + I_2$$


$$Y_0 = I_7 + I_5 + I_3 + I_1$$

  

Priority Encoders

- The operation of the priority encoder is such that *if two or more* inputs are equal to 1 at the same time, the input having the *highest* priority will take precedence.
- V is a *valid* bit indicator, that is set to 1 when one or more inputs are equal to 1


| I_3 | I_2 | I_1 | I_0 | Y_1 | Y_0 | V |
|-------|-------|-------|-------|-------|-------|-----|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 0 | 0 | 1 |
| 0 | 0 | 1 | x | 0 | 1 | 1 |
| 0 | 1 | x | x | 1 | 0 | 1 |
| 1 | x | x | x | 1 | 1 | 1 |

 


$$Y_1 = I_3 + I_2$$

$$Y_0 = I_3 + \bar{I}_2 I_1$$


$$V = I_3 + I_2 + I_1 + I_0$$

 


Encoder / Decoder Pairs

 

Multiplexers


 


| S_1 | S_0 | Y |
|-------|-------|-------|
| 0 | 0 | I_0 |
| 0 | 1 | I_1 |
| 1 | 0 | I_2 |
| 1 | 1 | I_3 |


 


Multiplexers

2-to-1 MUX

 
 


4-to-1 MUX

  



Multiplexers

▣ Quad 2-to 1 Mux

  

Multiplexers


▣ Quadruple 2-to-1 MUX

 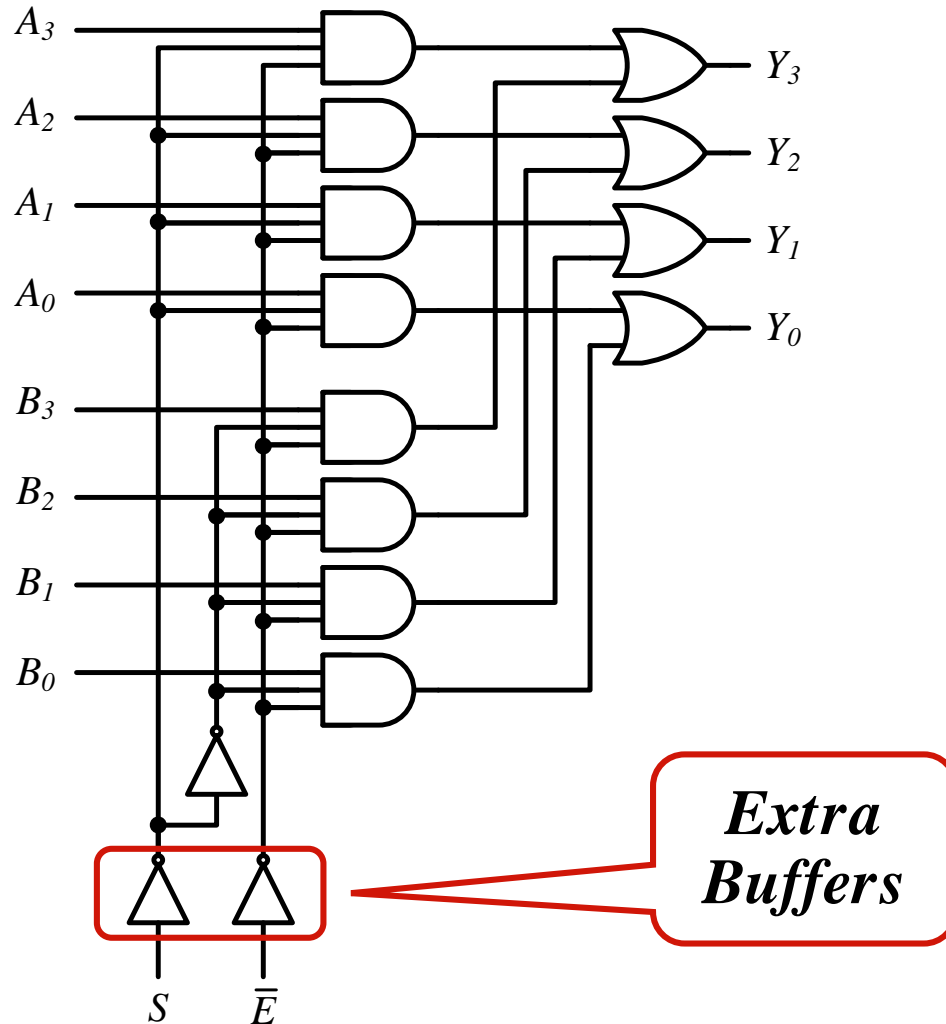

Implementation Using Multiplexers

■ Example

$$F(x, y) = \sum(0, 1, 3)$$

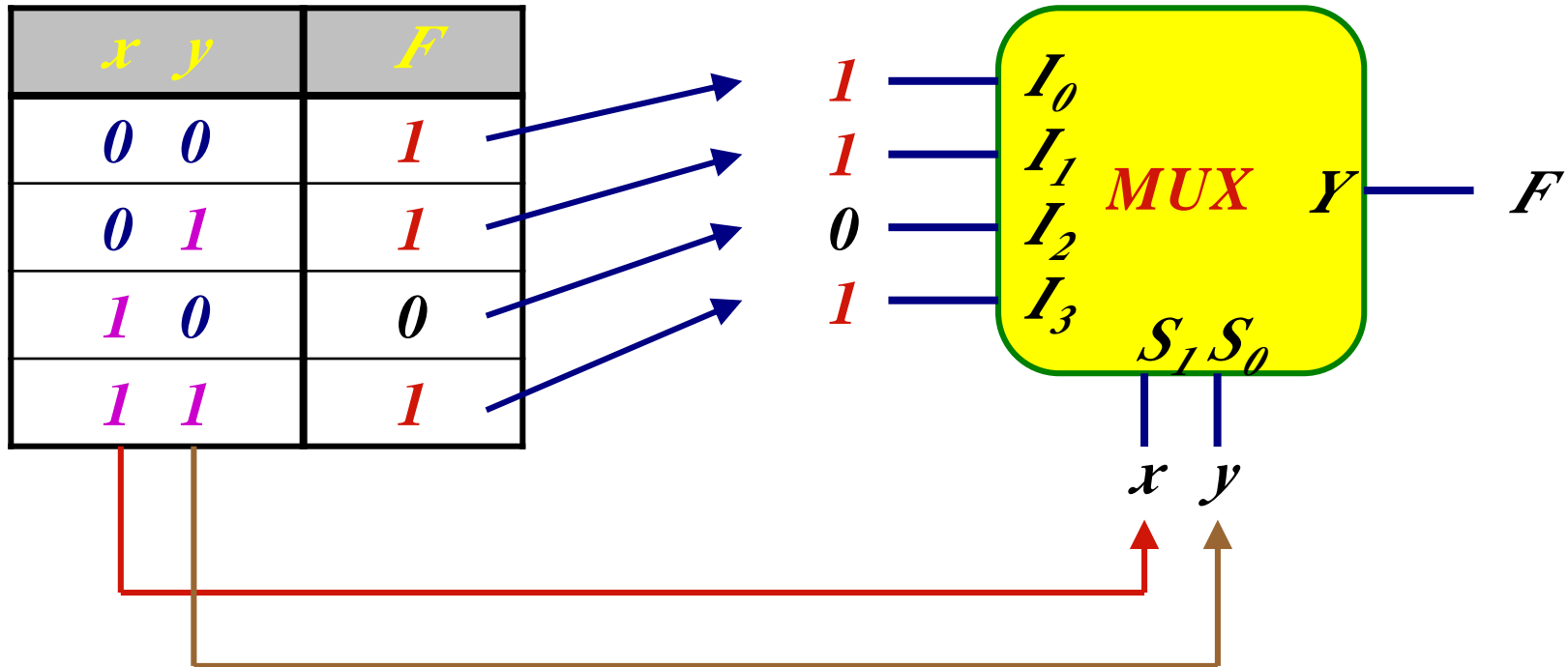


Implementation Using Multiplexers

Example

$$F(x, y, z) = \sum(1, 2, 6, 7)$$

| <i>x</i> | <i>y</i> | <i>z</i> | <i>F</i> |
|----------|----------|----------|----------|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |

 


Implementation Using Multiplexers

Example

Implement $F(x, y, z) = \sum(1, 2, 6, 7)$ using four-to-one Mux

| x | y | z | F |
|-----|-----|-----|-----|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |

 $\left. \begin{matrix} 0 & 0 & 0 \\ 0 & 0 & 1 \end{matrix} \right\} F = z$
 $\left. \begin{matrix} 0 & 1 & 0 \\ 0 & 1 & 1 \end{matrix} \right\} F = \bar{z}$
 $\left. \begin{matrix} 1 & 0 & 0 \\ 1 & 0 & 1 \end{matrix} \right\} F = 0$
 $\left. \begin{matrix} 1 & 1 & 0 \\ 1 & 1 & 1 \end{matrix} \right\} F = 1$




Implementation Using Multiplexers

Example


Implement $F(A, B, C, D) = \sum(1, 3, 4, 11, 12, 13, 14, 15)$ using 8-to-1 Mux.

| <i>A</i> | <i>B</i> | <i>C</i> | <i>D</i> | <i>F</i> | |
|----------|----------|----------|----------|----------|-----------------|
| 0 | 0 | 0 | 0 | 0 | } $F = D$ |
| 0 | 0 | 0 | 1 | 1 | |
| 0 | 0 | 1 | 0 | 0 | } $F = D$ |
| 0 | 0 | 1 | 1 | 1 | |
| 0 | 1 | 0 | 0 | 1 | } $F = \bar{D}$ |
| 0 | 1 | 0 | 1 | 0 | |
| 0 | 1 | 1 | 0 | 0 | } $F = 0$ |
| 0 | 1 | 1 | 1 | 0 | |
| 1 | 0 | 0 | 0 | 0 | } $F = 0$ |
| 1 | 0 | 0 | 1 | 0 | |
| 1 | 0 | 1 | 0 | 0 | } $F = D$ |
| 1 | 0 | 1 | 1 | 1 | |
| 1 | 1 | 0 | 0 | 1 | } $F = 1$ |
| 1 | 1 | 0 | 1 | 1 | |
| 1 | 1 | 1 | 0 | 1 | } $F = 1$ |
| 1 | 1 | 1 | 1 | 1 | |



 


Multiplexer Expansion

8-to-1 MUX using Dual 4-to-1 MUX

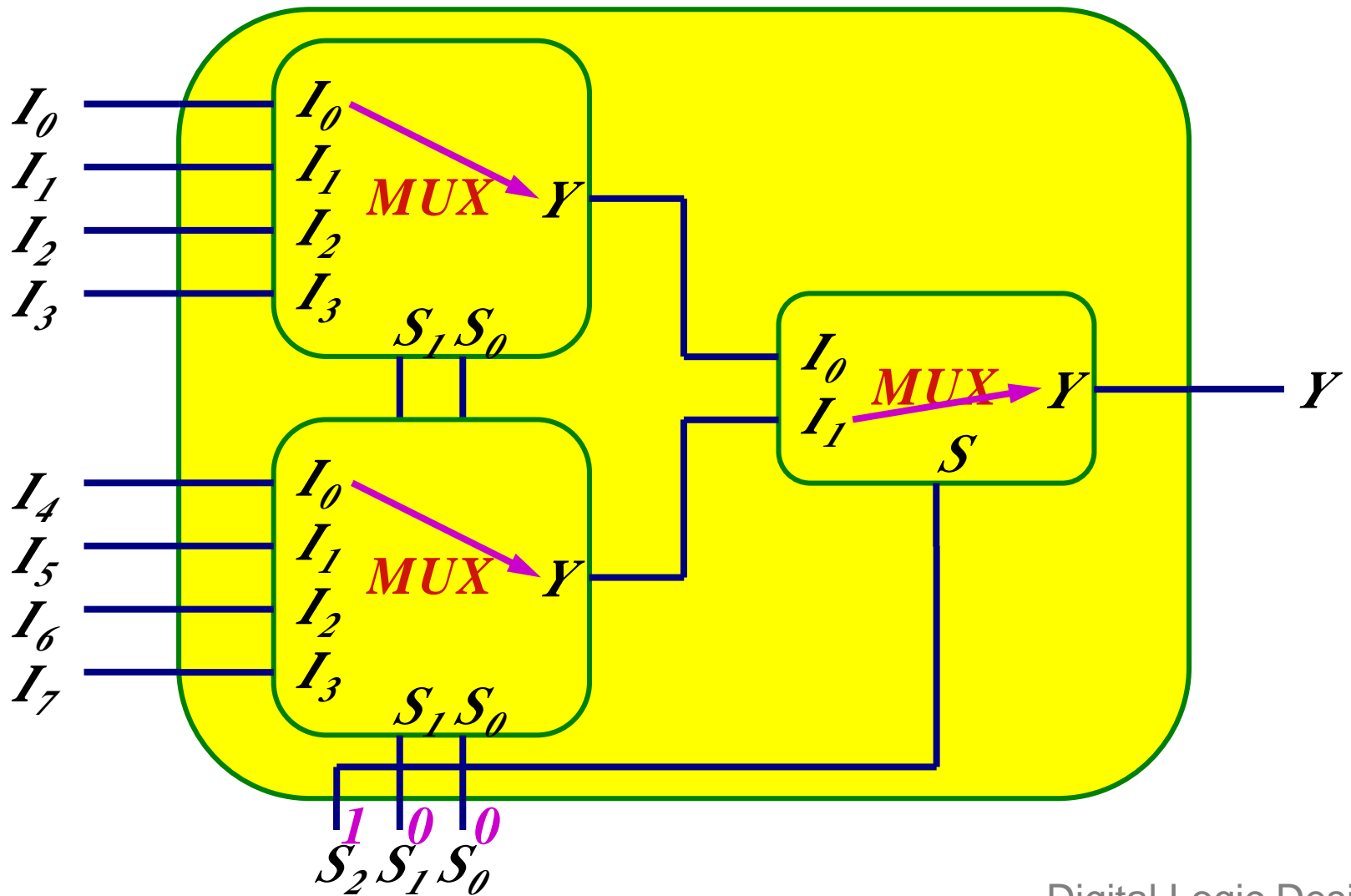


DeMultiplexers

  
 


| S_1 | S_0 | Y_3 | Y_2 | Y_1 | Y_0 |
|-------|-------|----------|----------|----------|----------|
| 0 | 0 | 0 | 0 | 0 | <i>I</i> |
| 0 | 1 | 0 | 0 | <i>I</i> | 0 |
| 1 | 0 | 0 | <i>I</i> | 0 | 0 |
| 1 | 1 | <i>I</i> | 0 | 0 | 0 |


Multiplexer / DeMultiplexer Pairs

 

DeMultiplexers vs Decoders

  

| S_1 S_0 | Y_3 | Y_2 | Y_1 | Y_0 |
|-------------|-------|-------|-------|-------|
| 0 0 | 0 | 0 | 0 | I |
| 0 1 | 0 | 0 | I | 0 |
| 1 0 | 0 | I | 0 | 0 |
| 1 1 | I | 0 | 0 | 0 |

 


| E | I_1 I_0 | Y_3 Y_2 Y_1 Y_0 |
|-----|-------------|-------------------------|
| 0 | x x | 0 0 0 0 |
| 1 | 0 0 | 0 0 0 I |
| 1 | 0 1 | 0 0 I 0 |
| 1 | 1 0 | 0 I 0 0 |
| 1 | 1 1 | I 0 0 0 |




Three-State Gates

Tri-State Buffer

 


| C | A | Y |
|-----|-----|-------------|
| 0 | x | <i>Hi-Z</i> |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

 


Graphic symbol for a three-state buffer

Tri-State Inverter

 


Three-State Gates

 


| C | D | Y |
|-----|-----|------|
| 0 | 0 | Hi-Z |
| 0 | 1 | B |
| 1 | 0 | A |
| 1 | 1 | ? |

Not Allowed

 

Three-State Gates

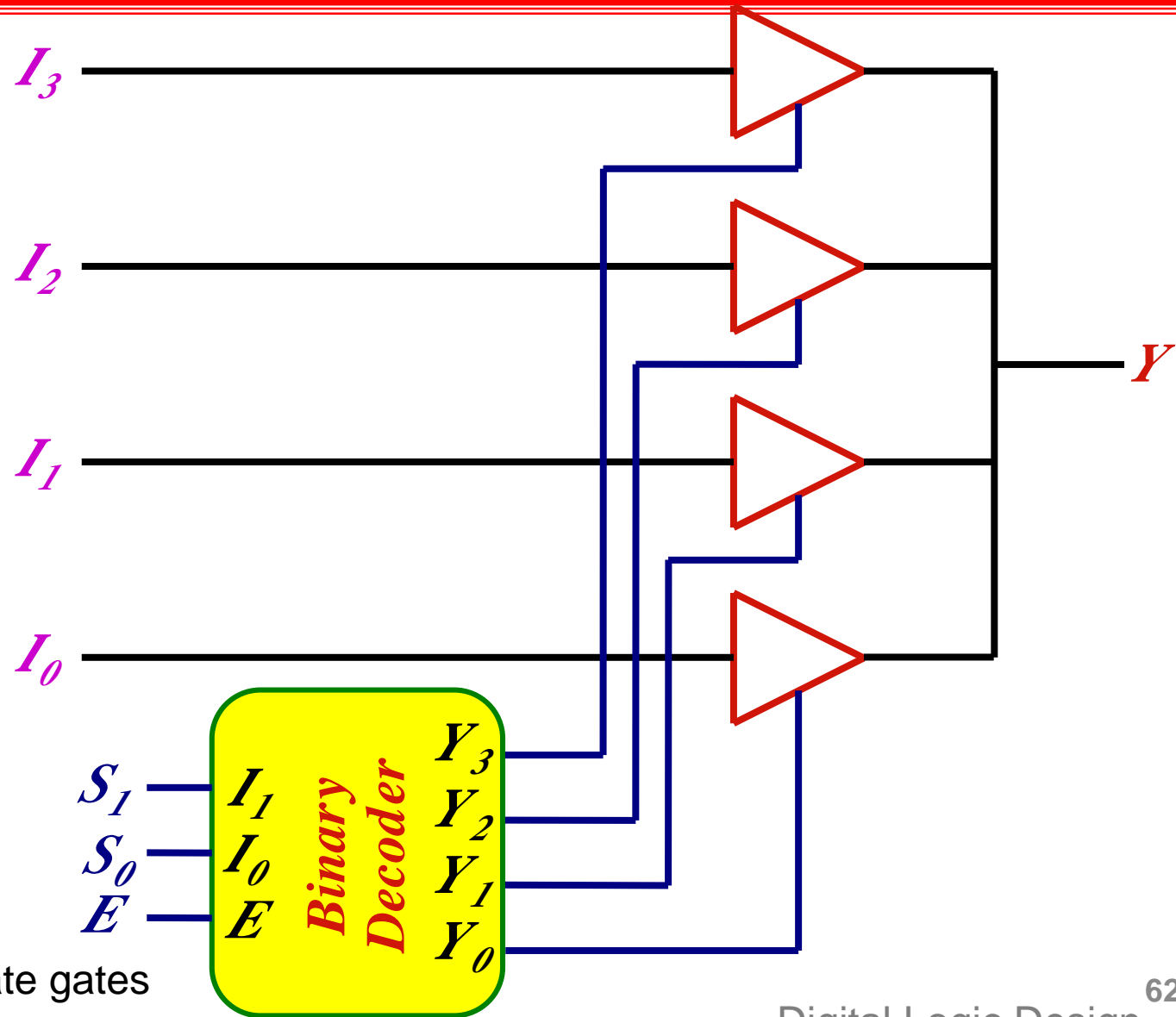

Decoder with three-state gates

Home Work (8)

Digital Design (**4th**)- Morris Mano-Page **175**

-Problems:

4.21

4.26

4.27

4.32

4.33

تم بحمد الله